

# EELE 250: Circuits, Devices, and Motors


Lecture 15

# Assignment Reminder

- Read 5.5-5.6, 6.2, AND 10.1 – 10.6 (diodes)
- Practice problems:
  - P5.63, P5.68, P5.77, P5.85
  - P6.23, P6.26
  - P10.7, P10.8, P10.37
- D2L Quiz #7 will be posted this week. It is due by 11AM on Monday 14 Oct.
- REMINDER: Lab #5 will be performed this week—be sure to do the pre-lab assignment calculations!  
There will be no EELE 250 labs *next* week.
- Exam #2: in class on Wednesday 23 Oct.

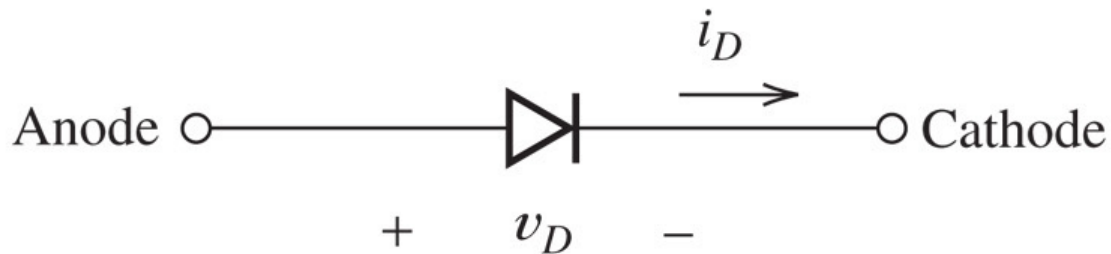
# Diodes

- Conceptually, a *diode* is an element that allows current to flow in one direction, but blocks current in the other direction.
- The fluid analogy: the diode is like a flapper valve in a pipe.
- Diode symbol:



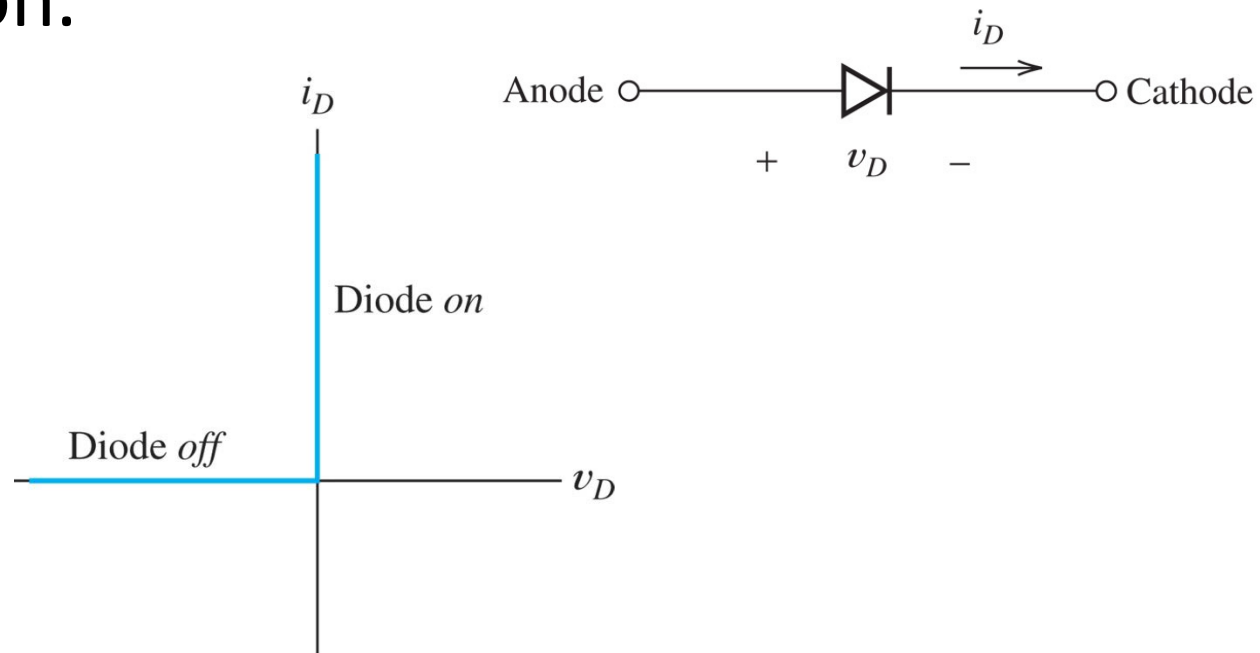
# The “ideal” diode model

- If a perfect diode could be made, it would act like a *short circuit* for one current direction and an *open circuit* for the other current direction.



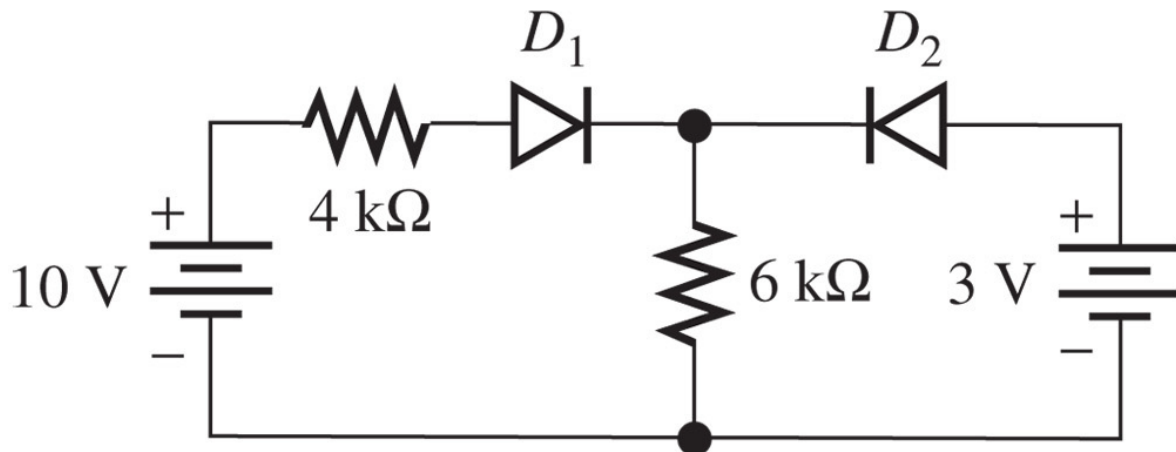
# Ideal diode model (cont.)

- We often use the ideal diode model to do a quick circuit assessment of whether a diode is “on” or “off” in a circuit. This is because diodes are *nonlinear* and therefore we cannot use linearity, superposition, etc.!



# The real diode model

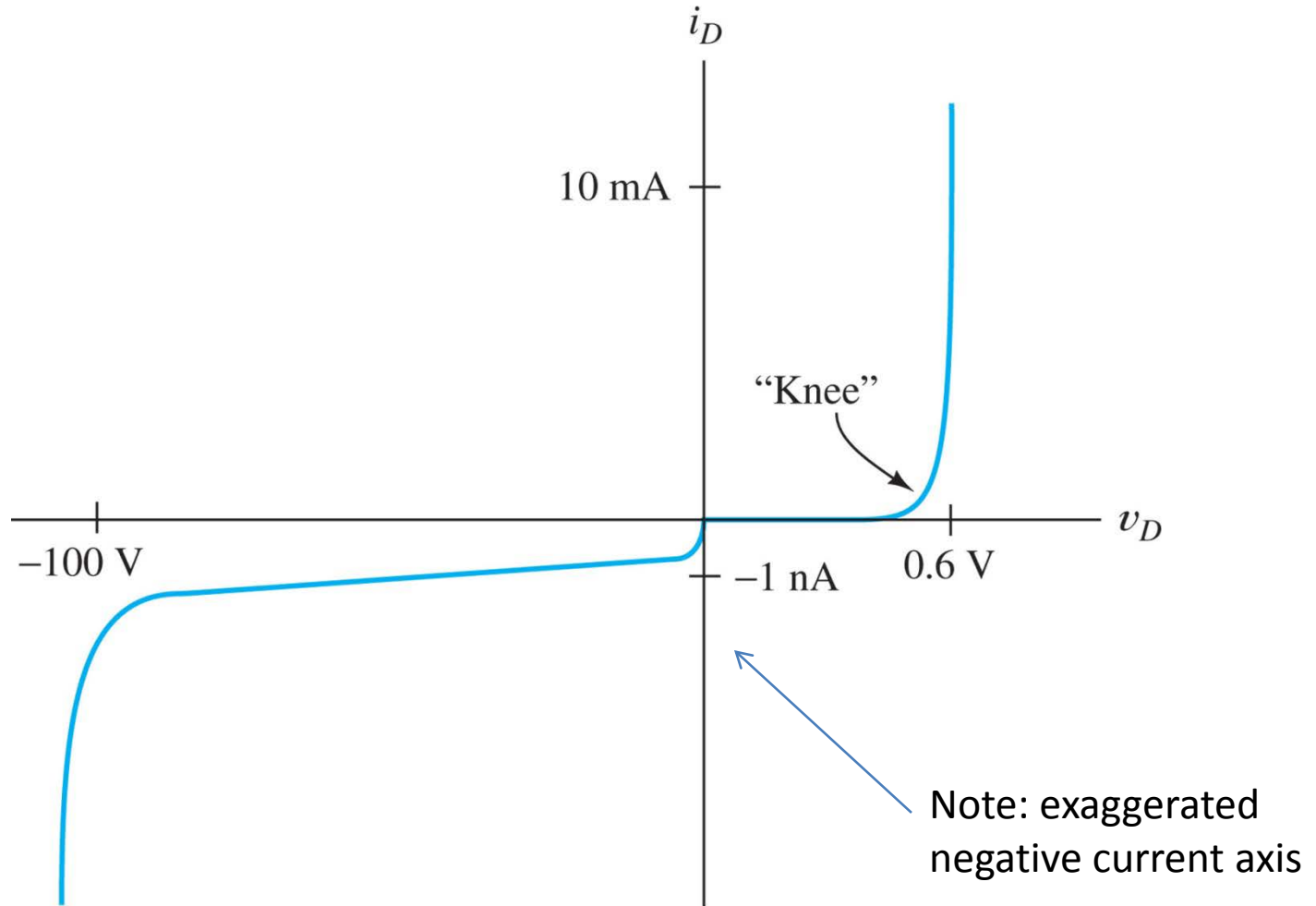

# Shockley Equation

- William Shockley, one of the inventors of the transistor, developed a mathematical model for semiconductor diodes.

- $$i_D = I_S \left( e^{\frac{v_D}{nV_T}} - 1 \right)$$



- $I_S$  is the *saturation current*

- $n$  is a coefficient ( $1 < n < 2$ ) that depends on the diode's design

- $V_t$  is the thermal voltage ( $kT/q$ ), about 26mV
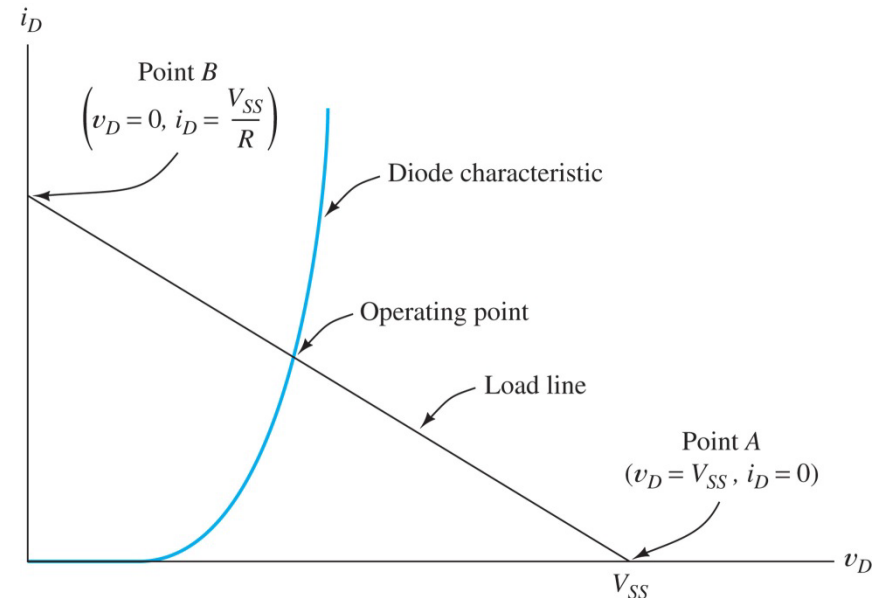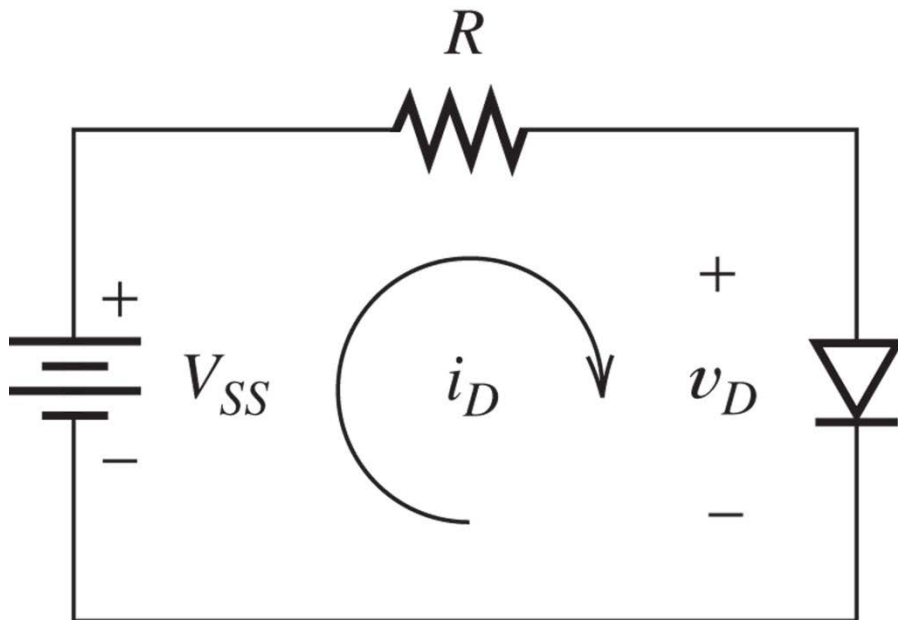
# Diode circuit analysis

- Diodes are nonlinear, as is clear from the Shockley equation.
- Equation solutions require nonlinear or iterative techniques.





# Frequency Response

- Recall:


$$Z_L = j\omega L$$

$$Z_C = 1 / j\omega C$$

- Low frequency,  $|Z_L| \rightarrow \text{zero}$ ,  $|Z_C| \rightarrow \text{infinity}$
- High frequency,  $|Z_L| \rightarrow \text{infinity}$ ,  $|Z_C| \rightarrow \text{zero}$
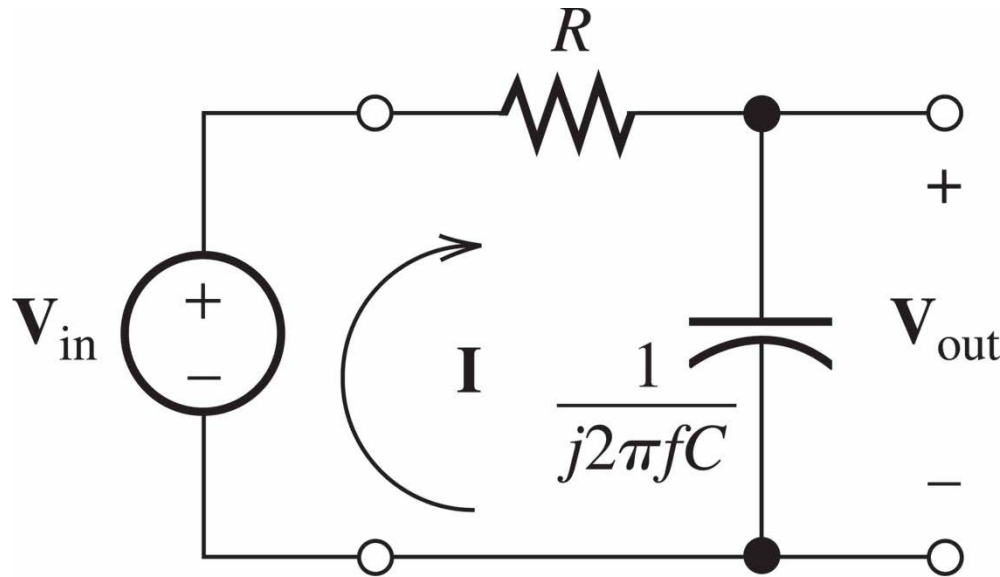
# “Low Pass” Filter

- A circuit that allows low frequencies to pass through and attenuates high frequencies



- $V_{out} = V_{in} \cdot Z_c / (R + Z_c) = V_{in} / (1 + j2\pi fRC)$

# Low Pass (cont.)



- $V_{out} = \frac{V_{in}}{(1+j2\pi fRC)}$
- As  $f \rightarrow$  zero,  $V_{out} \approx V_{in}$
- As  $f \rightarrow$  big,  $V_{out} \approx V_{in}/j2\pi fRC \approx$  zero
  
- $|V_{out}| = \frac{|V_{in}|}{\sqrt{1+(2\pi fRC)^2}}$
- $\angle V_{out} = -\arctan(2\pi fRC)$

# Where have we seen $R \cdot C$ before?

- The *time constant* came up when we looked at RC transient analysis:  $t_c = R \cdot C$
- If we define  $\omega_b = 1/(RC)$ , or  $f_b = 1/(2\pi RC)$ , then  $RC = 1/(2\pi f_b)$
- $$V_{out} = \frac{V_{in}}{(1+j2\pi f RC)} = \frac{V_{in}}{1+j(2\pi f / 2\pi f_b)} = \frac{V_{in}}{1+j(f/f_b)}$$
- When  $f = f_b$ ,  $V_{out} = V_{in}/(1+j1) = V_{in}/(0.707 \angle 45^\circ)$


# Magnitude and Phase

- $V_{out} = \frac{V_{in}}{(1+j2\pi fRC)} = \frac{V_{in}}{1+j(2\pi f/2\pi f_b)} = \frac{V_{in}}{1+j(f/f_b)}$
- When  $f = f_b$ ,  $V_{out} = V_{in}/(1+j1) = V_{in}/(0.707 \angle 45^\circ)$
- $|V_{out}| = \frac{|V_{in}|}{\sqrt{1+(f/f_b)^2}}$ ,  $\angle V_{out} = -\arctan(f/f_b)$

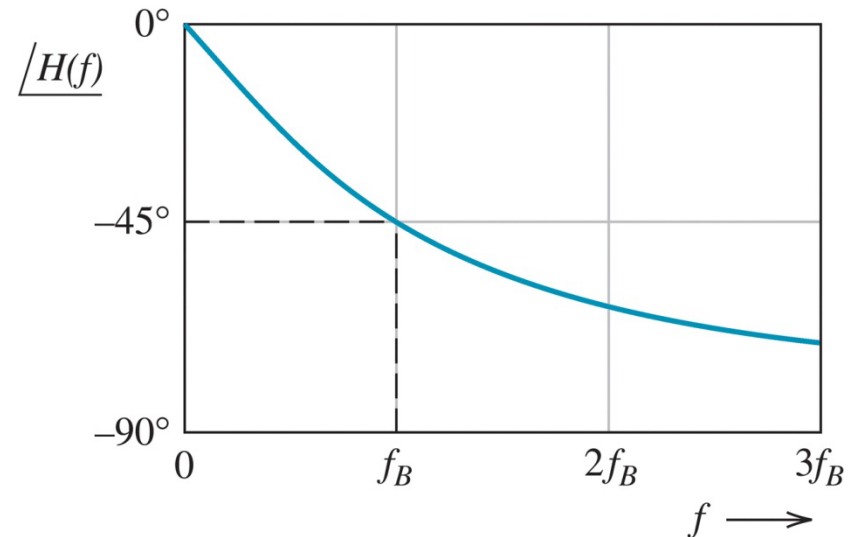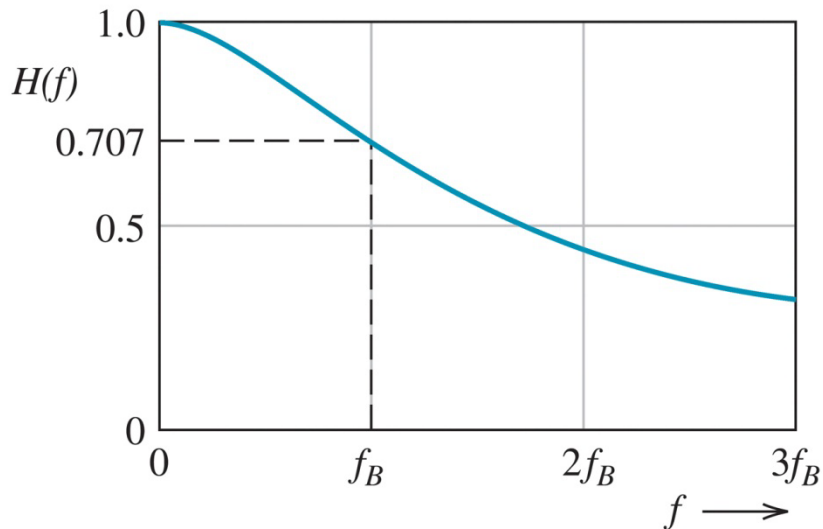

# High Pass Filter

- Interchange R and C:


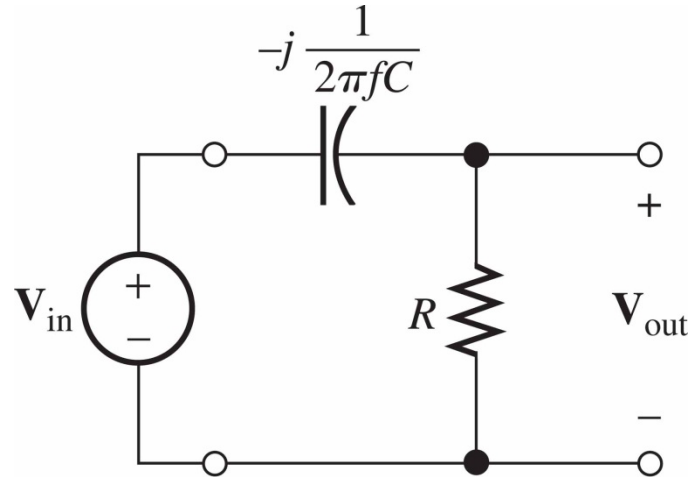


- Low frequencies are blocked, high frequencies are passed through to  $v_{out}$

# High Pass (cont.)

- As we did for Low Pass, we can define

$$f_b = 1/(2\pi RC)$$

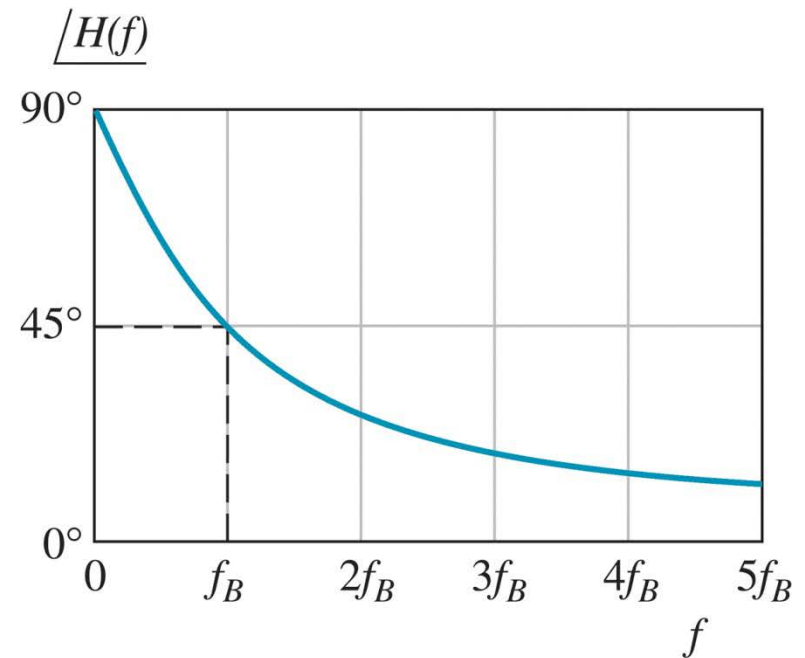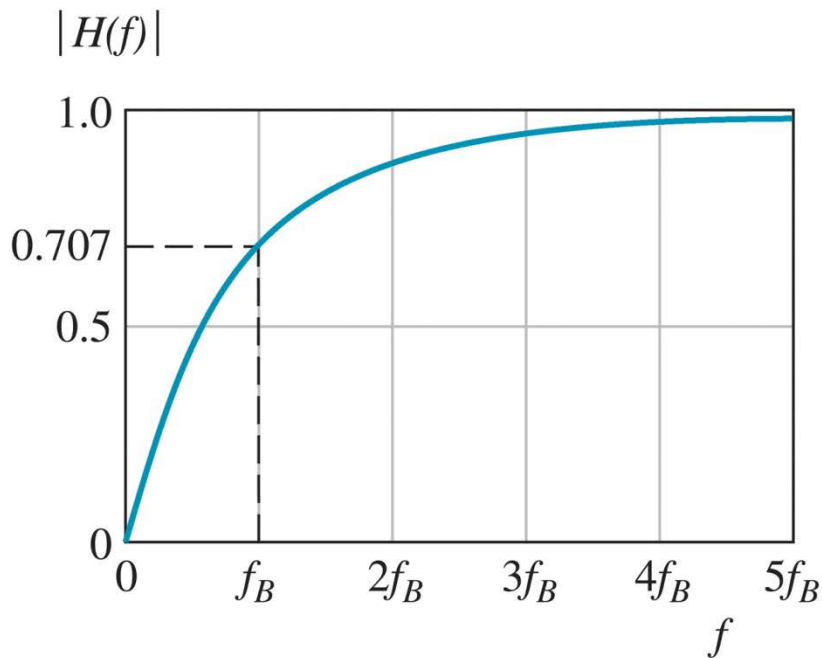

# Frequency-selective Filters

- Bass/Treble control for a stereo
- Remove high frequency or low frequency noise
- Smooth out (low pass) or accentuate (high pass) variations in a signal
- Signal processing: high pass acts like a *differentiator* ( $d/dt$ ), while low pass acts like an *integrator* ( $\int dt$ )