


# EELE 250: Circuits, Devices, and Motors

Op Amps (cont.)

# Assignment Reminder


- Read 14.7 and 14.9; also read 5.7 (3 phase)
- Practice Problems:
  - P14.19, P14.20, P14.22, P14.23, P14.32
- Lab #7 this week. Note that there is a design to be done in the prelab. Lab notebooks collected by Friday afternoon.
- D2L Quiz posted later this week
- Exam #3: Friday 15 Nov.

# Clicker quiz

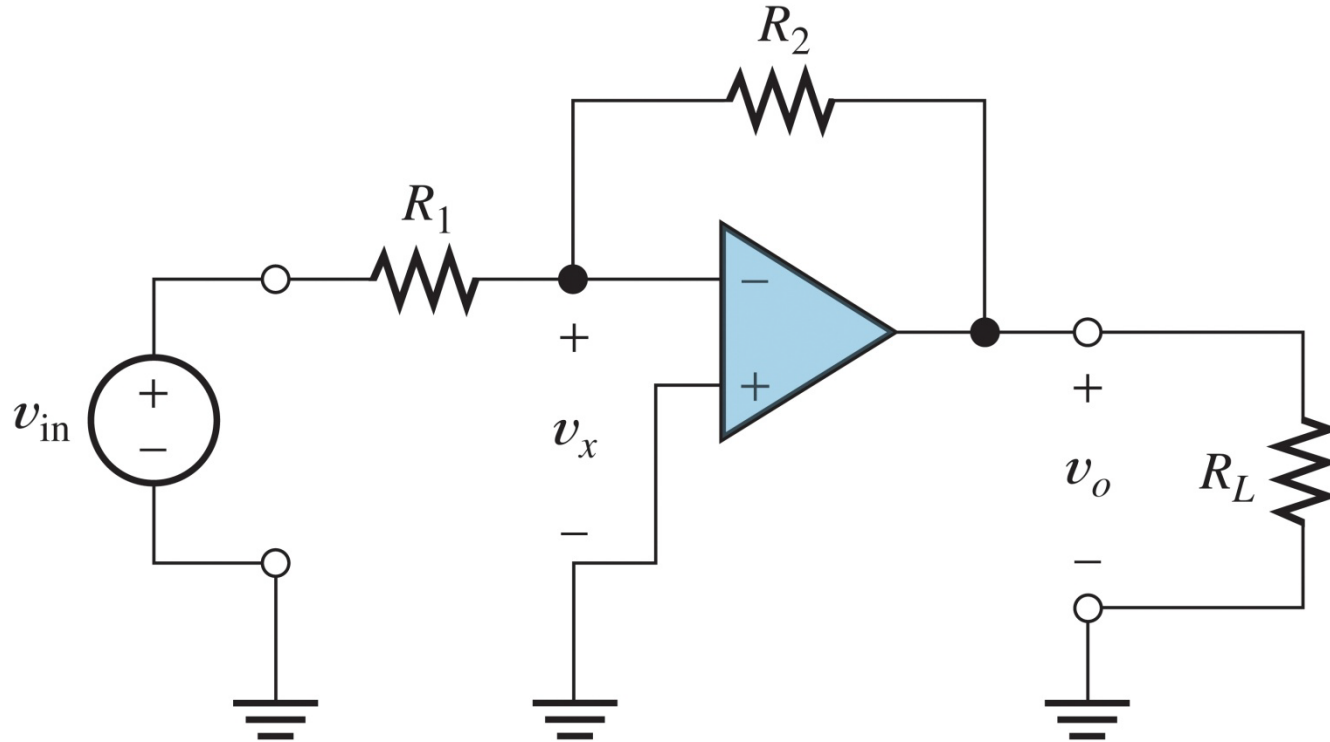


- (a)  $V_o = -R_L V_{in}$
- (b)  $V_o = -V_{in}$
- (c)  $V_o = -(R_2/R_1) V_{in}$
- (d)  $V_o = -(R_1/R_2) V_{in}$
- (e)  $V_o = (1+R_2/R_1) V_{in}$

# Clicker quiz

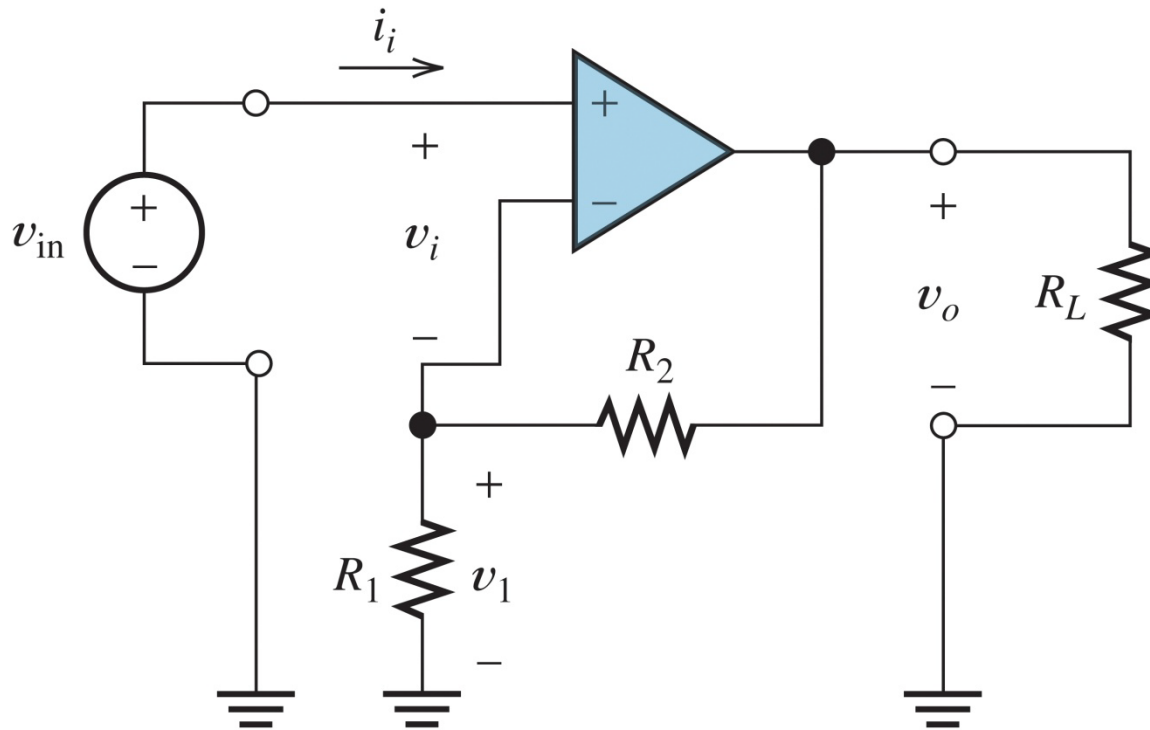

- (a)  $V_o = -R_L V_{in}$
- (b)  $V_o = -V_{in}$
- (c)  $V_o = -(R_2/R_1) V_{in}$
- (d)  $V_o = -(R_1/R_2) V_{in}$
- (e)  $V_o = (1+R_2/R_1) V_{in}$


# Clicker quiz

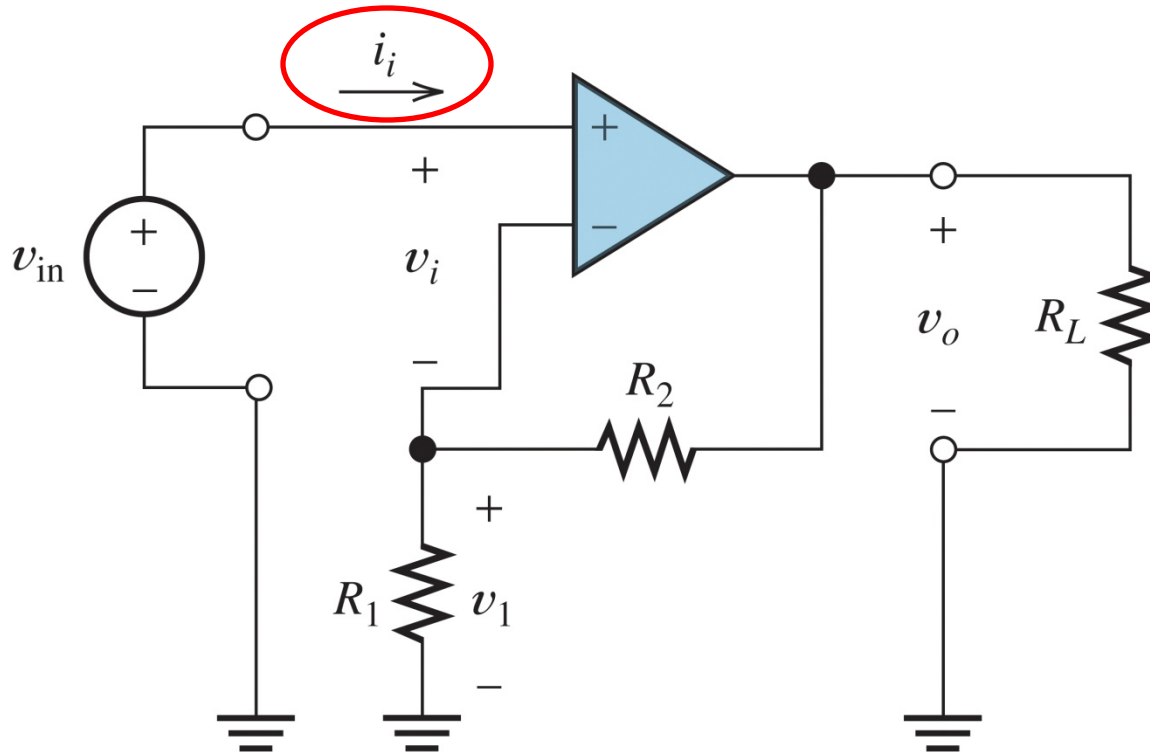

Assuming the ideal op amp model, what is  $i_i$ ?

- (a)  $i_i = V_o/R_L$
- (b)  $i_i = V_1/R_1$
- (c)  $i_i = V_{in}/R_1$
- (d)  $i_i = 0$


# Clicker quiz

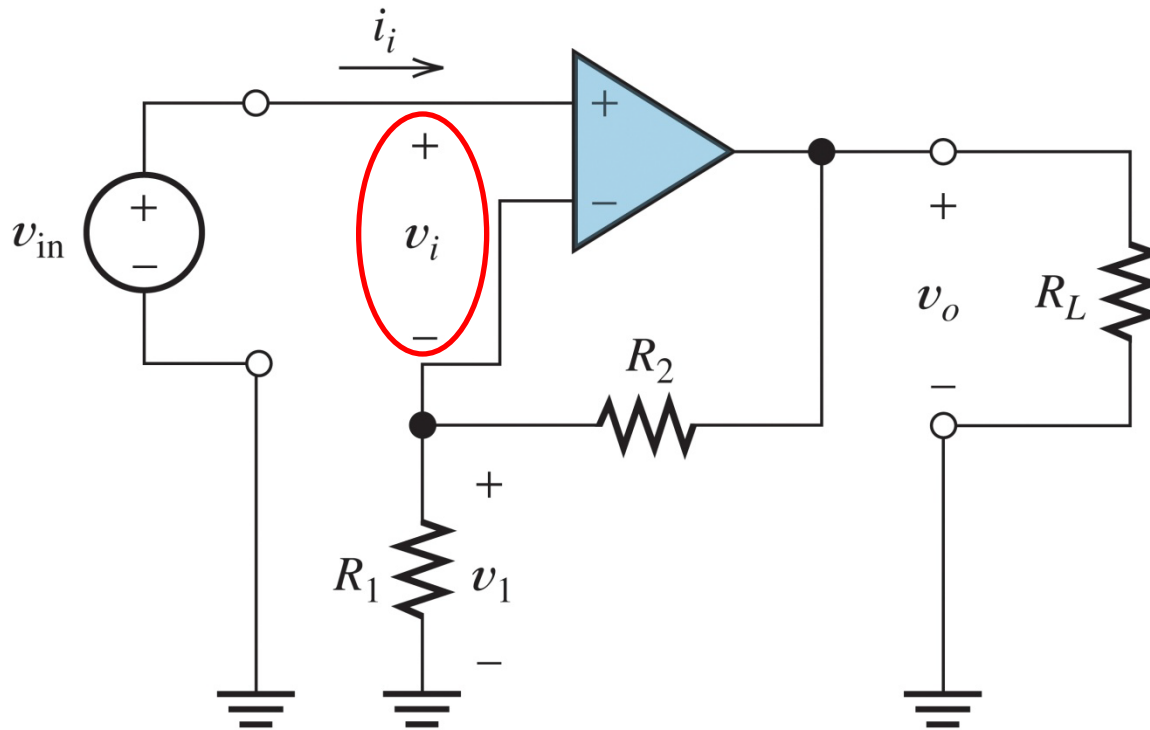

Assuming the ideal op amp model, what is  $v_i$ ?

- (a)  $v_i = 0$
- (b)  $v_i = v_{in}$
- (c)  $v_i = -v_{in}$
- (d)  $v_i = v_o$

# Clicker quiz

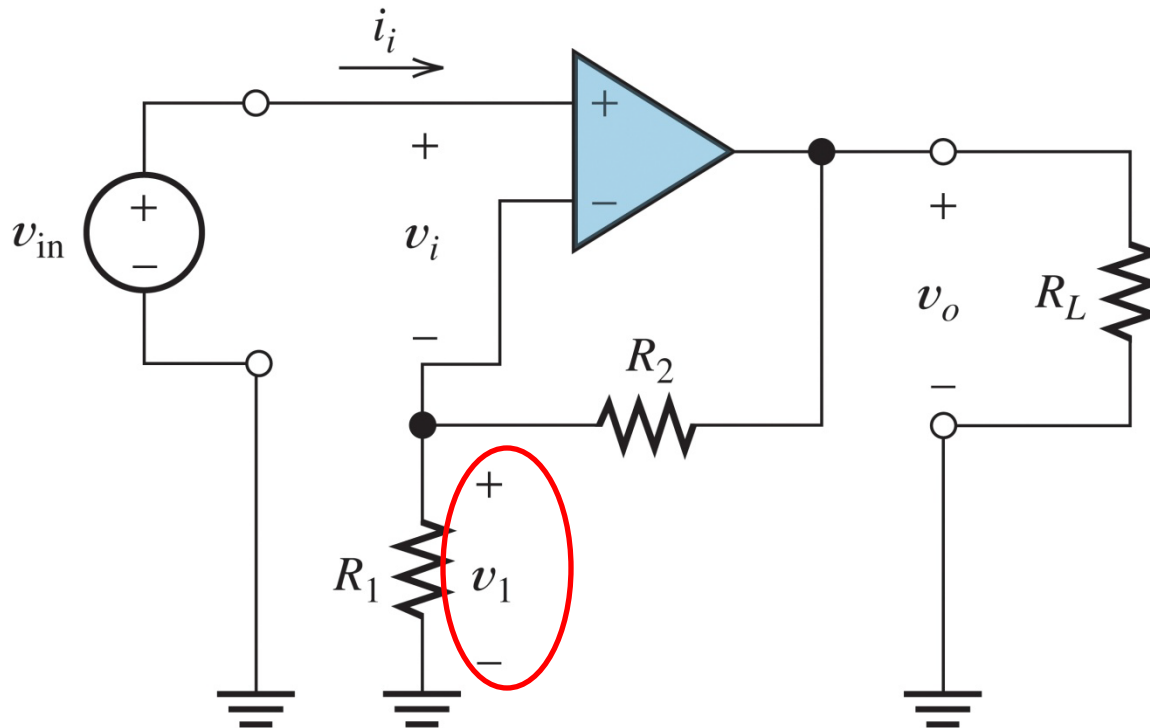

Assuming the ideal op amp model, what is  $v_1$ ?

- (a)  $v_1 = v_{in} (R_1 / (R_1 + R_2))$
- (b)  $v_1 = v_{in}$
- (c)  $v_1 = -v_{in}$
- (d)  $v_1 = v_o$

# Design with Op Amps



- Typical op amp circuit design involves selecting external resistors to achieve a particular voltage gain, current gain, etc.
- Design involves selecting the best solution from several possible choices. This usually entails tradeoffs and compromises.
- Often choose basic circuits as building blocks:
  - Inverting and non-inverting configuration
  - Voltage follower
  - Summer



# Design Example

- We would like to create a control voltage to steer a solar array to point at the sun.
- Two optical sensors: sensors produce a current proportional to how strongly they are illuminated.
  - If the left sensor is illuminated more than the right, we need a proportional POSITIVE voltage.
  - If the right sensor is illuminated more than the left, we need a proportional NEGATIVE voltage.

# Design Example (cont.)

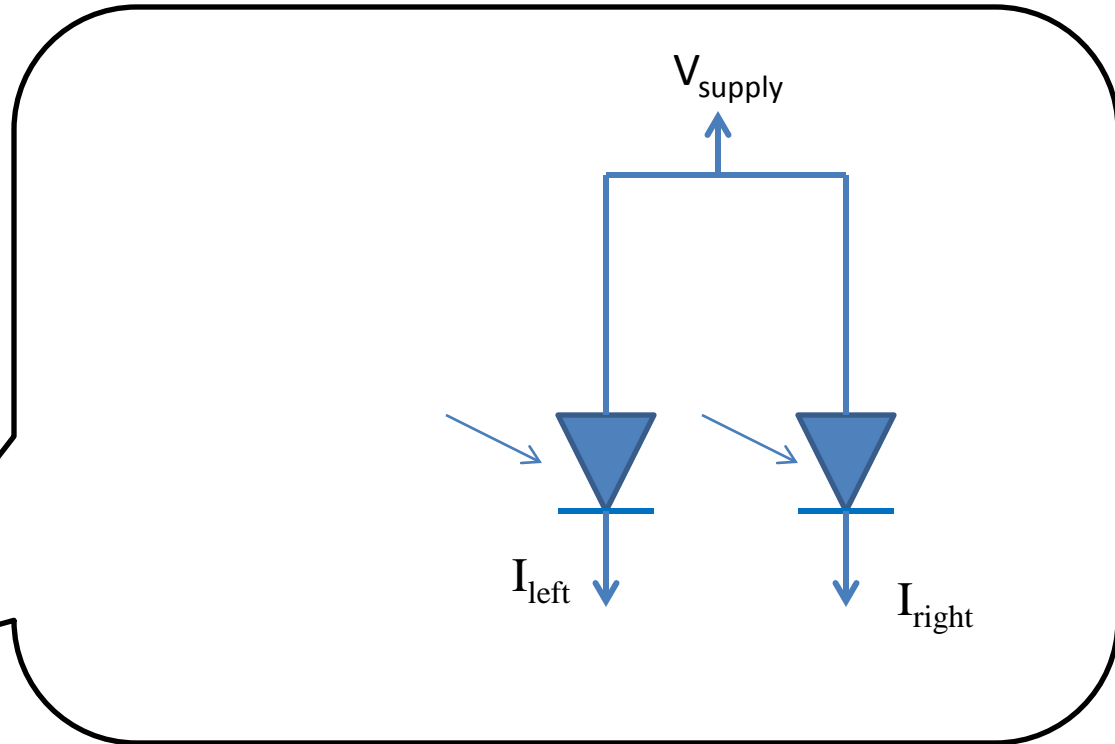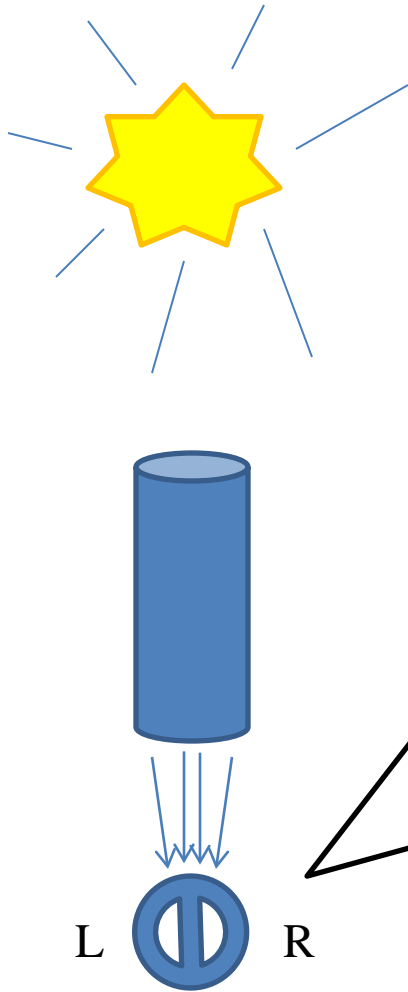

# Design Example (cont.)

- Interpretation: We want a circuit that will create a voltage proportional to  $(I_{\text{left}} - I_{\text{right}})$
- One idea: convert the currents into voltages, subtract them, and then amplify the result
- Current to voltage converter?
- Summer?

